

EL 6463 – Homework 2

Name: Xinran Tang

NYU ID Number: N10257233

Net ID: xt2191

Link to the video:

<https://drive.google.com/file/d/1k1Cl0AqQf0EhZrTYzOGWji9IVgErfbSA/view?usp=sharing>

Task1: design


Because the speed of 16bit counter is too fast, the change of counter cannot be seen from the change of LED, so in this project, the last 16 bits of a 42bit counter are intercepted to control the blinking of LED.

Task 2: functional simulation of each of the 2 counters

- functional simulation of the CounterA: Verilog, Counts UP


case 1:

clk: 100MHz, rst=0, cnt_en=1

 


case 2:

clk: 100MHz, rst=1, cnt_en=1

 


case 3:

clk: 100MHz, rst=1, cnt_en=0

 

case 4:


clk: 100MHz, rst=0, cnt_en=0

 

● functional simulation of the CounterB: VHDL, Counts DOWN


case 1:

clk: 100MHz, rst=0, cnt_en=1

 


case 2:

clk: 100MHz, rst=1, cnt_en=1

 


case 3:

clk: 100MHz, rst=1, cnt_en=0

 

case 4:


clk: 100MHz, rst=0, cnt_en=0

 

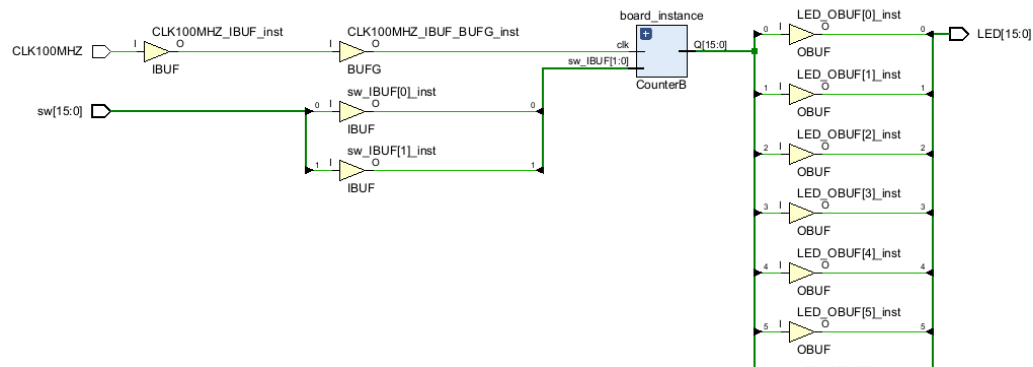
Task 3: Schematic of each of the 2 counters

The diagram has three input and one output. The counters use 100MHz input clock as an input clock. Then, use sw[0] to control the input active-high reset signal, use sw[1] to control the input enable signal for counting. Finally, get an 16bit output.


- **Schematic of the CounterA: Verilog, Counts UP**
In detail




Overall

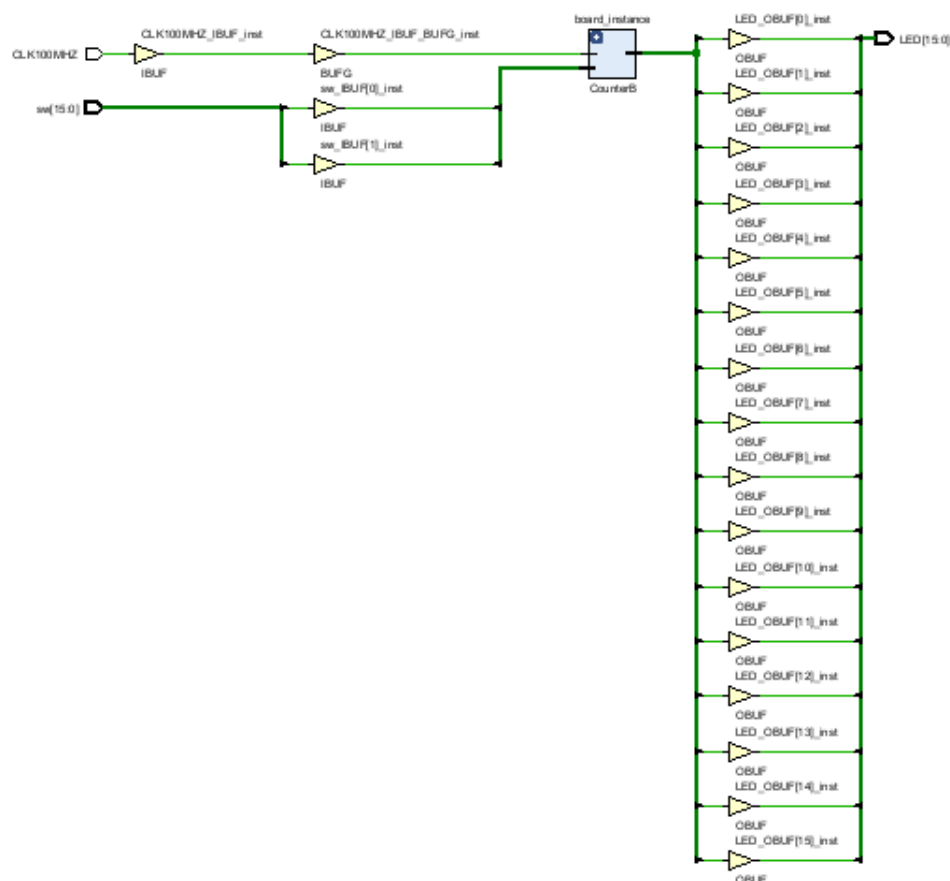

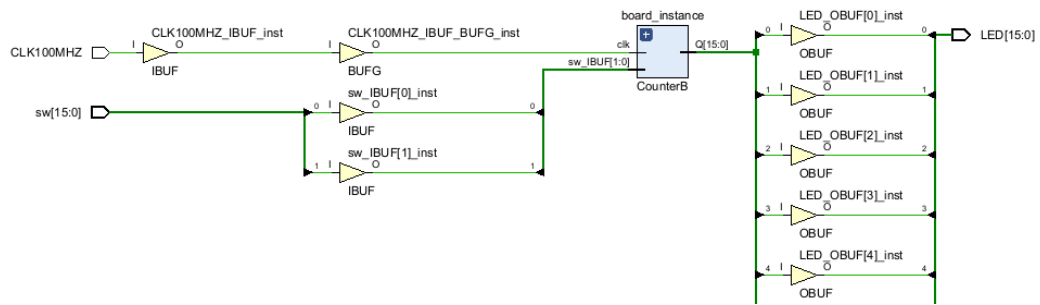- **Schematic of the CounterB: VHDL, Counts DOWN**
In detail



Overall

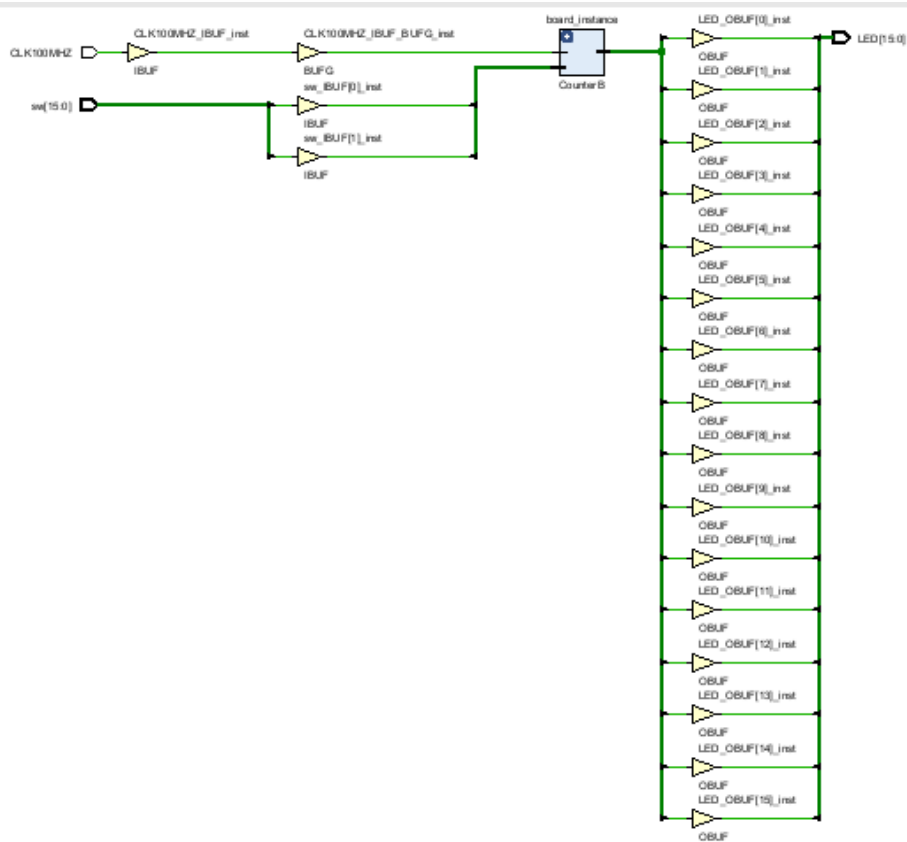

Difference between the Verilog and VHDL hardware

1. compared to VHDL, Verilog requires fewer lines of code to complete the same task
2. VHDL does not allow mixing or manipulating variables with different classes, while Verilog does